

Assignment #5 – Digital Logic Design I – Combinational Logic

CDA 3100, Computer Organization I

Problem 1 (40 points) Design a circuit that takes three bits X_2 , X_1 , X_0 , as input, and output one bit O as output. O is 1 if and only if $2 \leq X \leq 5$ when $X = (X_2, X_1, X_0)$ is read as an unsigned integer.

(a) Complete the truth table.

X_2	X_1	X_0	O
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b) Write down the sum-of-product form of the function without any simplification in the format as: $O = (X_2 \& X_1 \& X_0) \mid (\sim X_2 \& X_1 \& X_0) \mid \dots$ (this is NOT the answer).

$O =$

(c) Simplify the circuit using Karnaugh-map.

X2X1	00	01	11	10
X0				
0				
1				

(d) Write down the Verilog module for this circuit called module HW5P1 (X2, X1, X0, O).

(e) A Verilog code has been provided for this homework with an empty HW5P1 module. Please replace this module with your module and run simulation. Copy and paste the waveform **only related to this problem** here. One way to copy and paste is: 1) print screen, 2) paste the screen to the windows paint program, 3) crop the waveform, and 4) paste it here.

Problem 2 (40 points) Design a circuit that takes three bits A, B, S as input, and output one bit O as output. If $S=0$, $O=A \oplus B$. If $S=1$, $O=A \& B$.

(a) Complete the truth table.

S	A	B	O
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b) Write down the sum-of-product form of the function without any simplification in the format as: $O = (A \& B \& S) \vee (A \& B \& \sim S) \vee \dots$ (this is NOT the answer)

O =

(c) Simplify the circuit using Karnaugh-map.

SA \ B	00	01	11	10
0				
1				


(d) Write down the Verilog module for this circuit called module HW5P2 (S,A,B,O).

(e) A Verilog code has been provided for this homework with an empty HW5P2 module. Please replace this module with your module and run simulation. Copy and paste the waveform **only related to this problem** here.

Problem 3 (10 points) Design a comparator which has 6 input bits, A_2, A_1, A_0 and B_2, B_1, B_0 , and one output bit O . Let $A=(A_2, A_1, A_0)$ and $B=(B_2, B_1, B_0)$, and regard them as unsigned integers. If $A>B$, $O=1$; else $O=0$. **Please write down the logic function as your answer. No Verilog code or simulation is needed.** Hint: This problem should be solved by analyzing the underlying logic and no Karnaugh-map is needed. For example, if $A_2=1$ and $B_2=0$, O must be 1 and there is no need to check the values of other input bits.

Problem 4 (10 points) We talked about multiplexors in the class. A 4-1 multiplexor has 6 inputs $S1$, $S0$, $d3$, $d2$, $d1$, and $d0$, and has one output O . It works as follows. If $S1S0=00$, $O=d0$. If $S1S0=01$, $O=d1$. If $S1S0=10$, $O=d2$. If $S1S0=11$, $O=d3$. Show how to use **only** one 4-1 multiplexor to implement function $F(A,B,C)$ with truth table shown below. No any other gates should be used, including the inverter; meaning that the inputs to the 4-1 multiplexor can only be from A , B , C , 0 , or 1 . **Please finish the following figure, showing each input of the 4-1 multiplexor is connected to which one among A , B , C , 0 , or 1 , as your answer.** No Verilog code or simulation is needed. For this problem, no Karnaugh-map is needed.

A	B	C	O
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 

The Verilog code that will be needed in this homework is:

http://ww2.cs.fsu.edu/~dennis/cda3100_summer_2013/homework/hwk5.v

Instructions about the Verilog Simulator can be found in slides Week8-day1.