


MIPS processor continued

Review

- Different parts in the processor should be connected appropriately to be able to carry out the functions.
- Connections depending on what we need
- Learnt R-type, lw, sw, beq


In Class Exercise Question

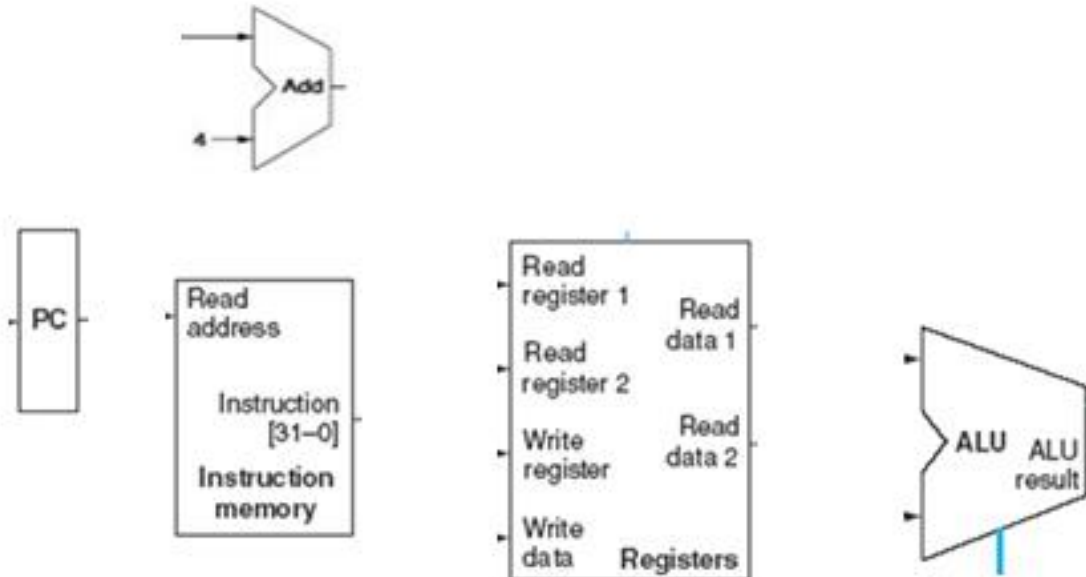- Design a simplified MIPS processor that supports **only** addi. Assume the control signals have been generated and only the data path needs to be designed.
 - addi \$rt, \$rs, imm
 - opcode (6 bits) rs (5 bits) rt (5 bits) imm (16 bits)




In Class Exercise Answer

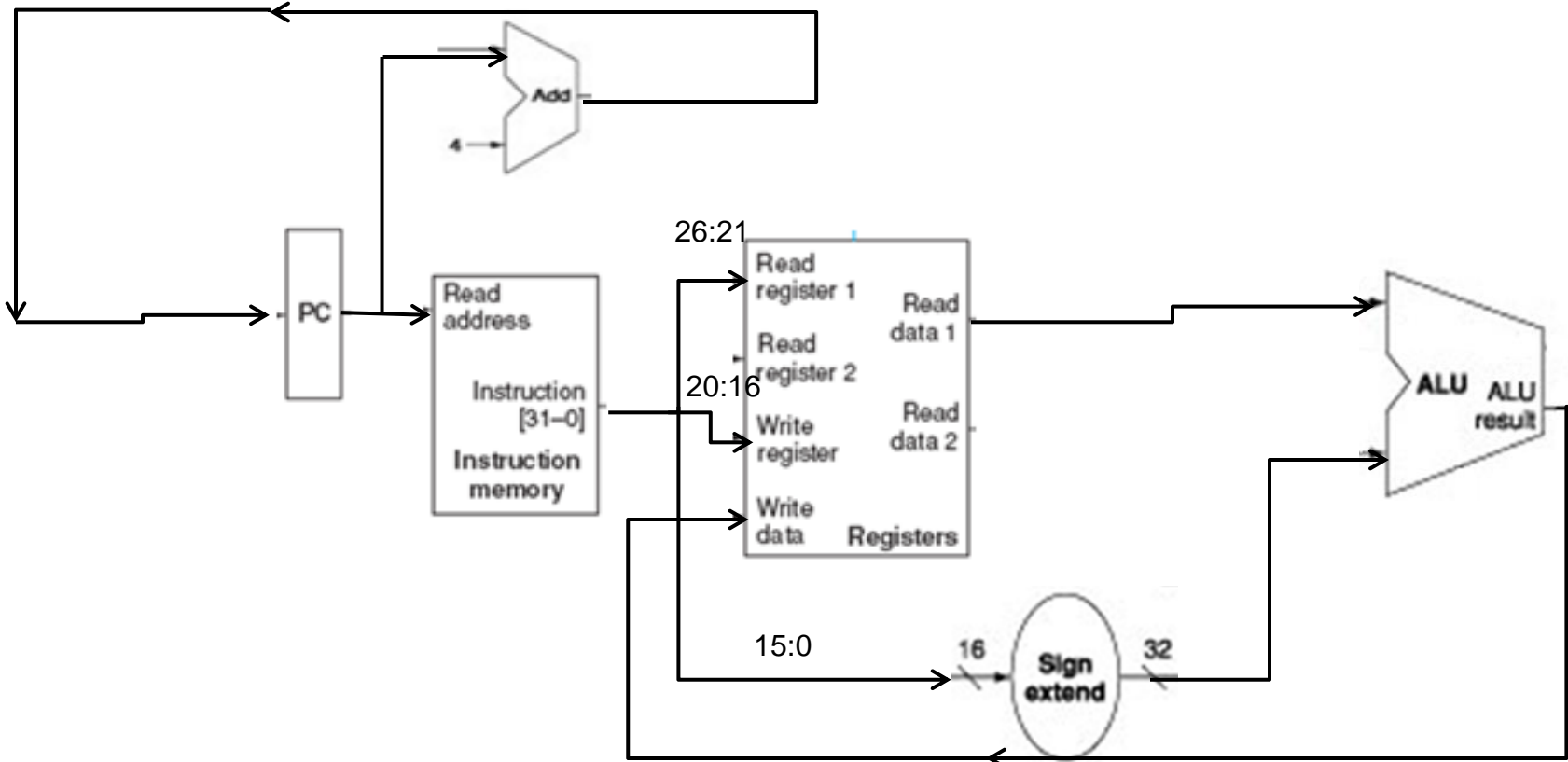
- Design a simplified MIPS processor that supports **only** addi. Assume the control signals have been generated and only the data path needs to be designed.
 - addi \$rt, \$rs, imm
 - opcode (6 bits) rs (5 bits) rt (5 bits) imm (16 bits)



lw & sw?

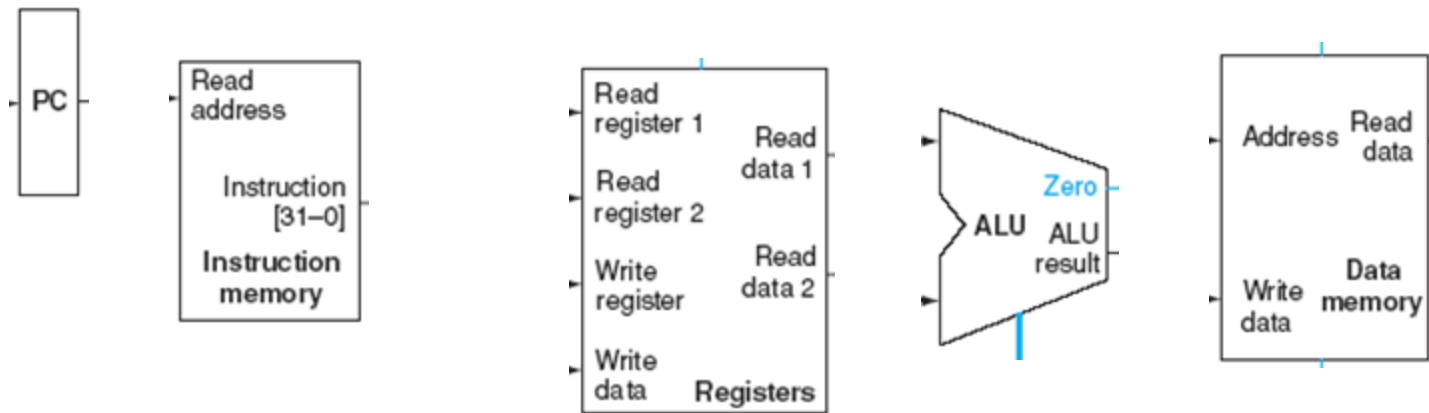


Data path only for lw and sw (answer)

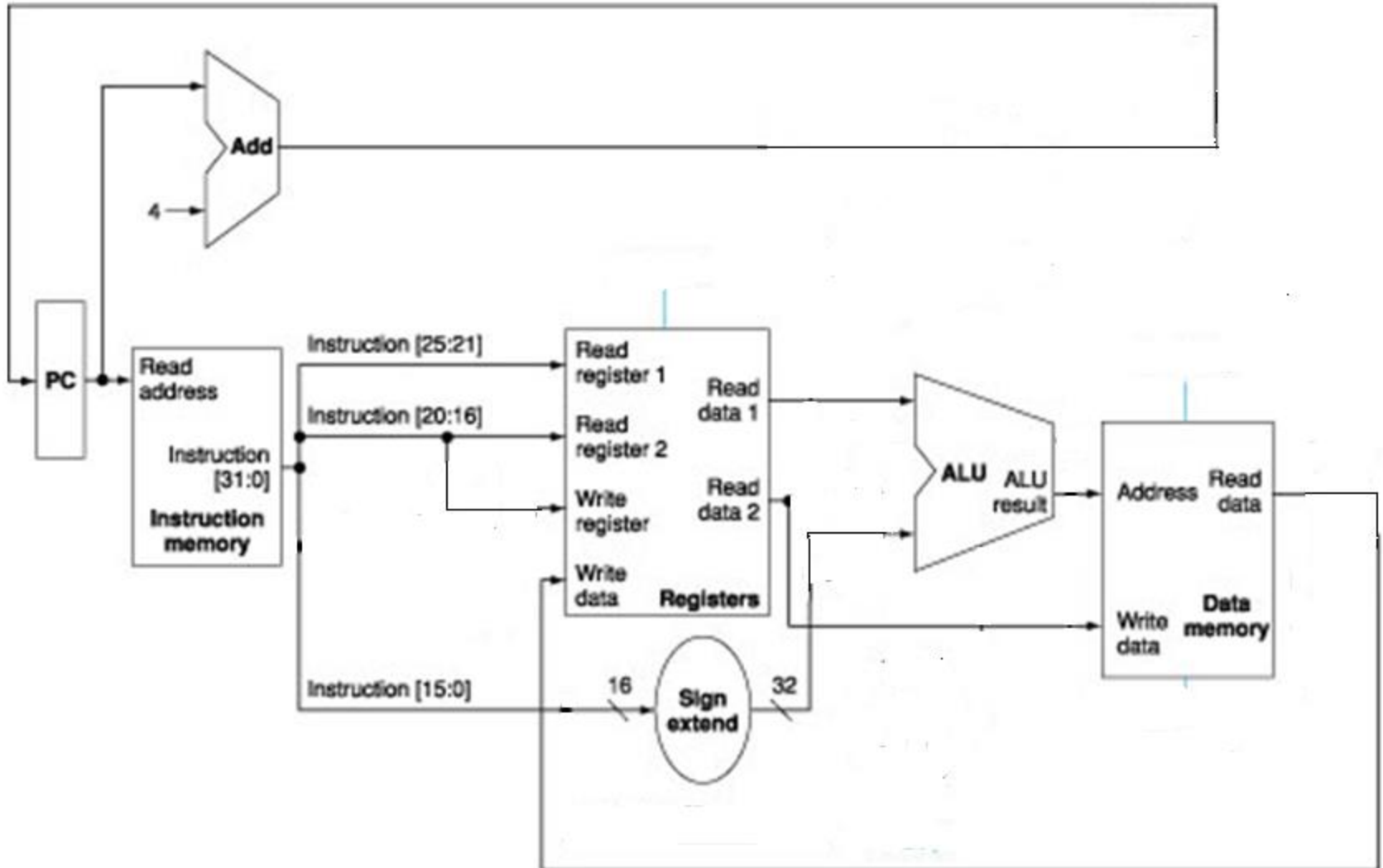


Data path for both R-type and memory-type instructions

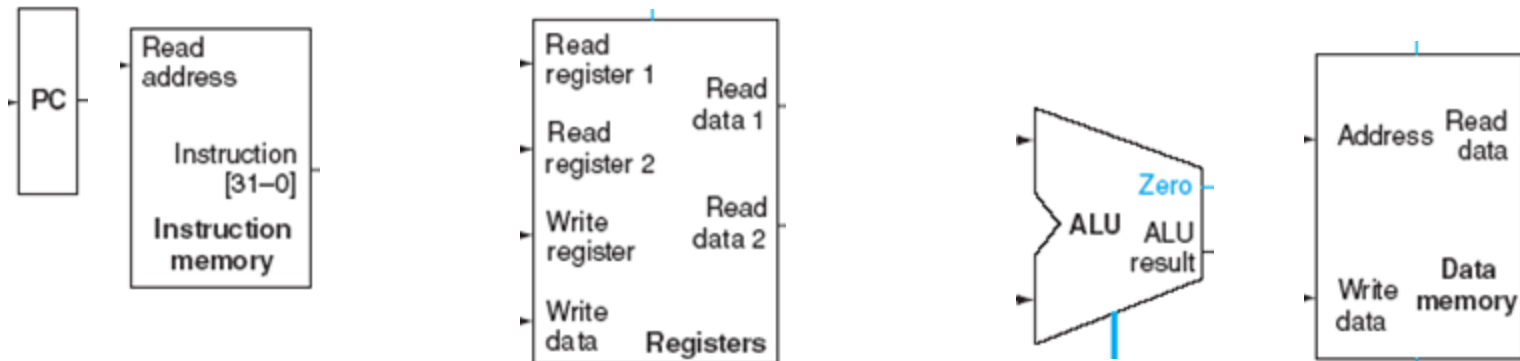add \$rd, \$rs, \$rt, format: opcode (6 bits) rs (5 bits) rt (5 bits) rd (5 bits) 00000 funct (6 bits)
lw \$rt, offset_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)
sw \$rt, offset_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)




Data path for both R-type and memory-type instructions

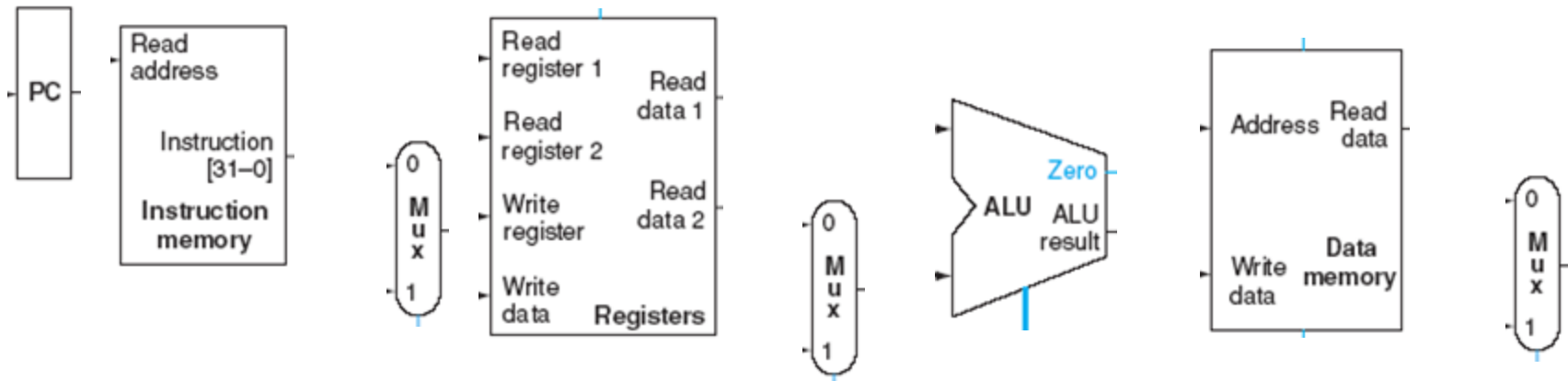
add \$rd, \$rs, \$rt, format: opcode (6 bits) rs (5 bits) rt (5 bits) rd (5 bits) 00000 funct (6 bits)
lw \$rt, offset_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)
sw \$rt, offset_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)




Answer

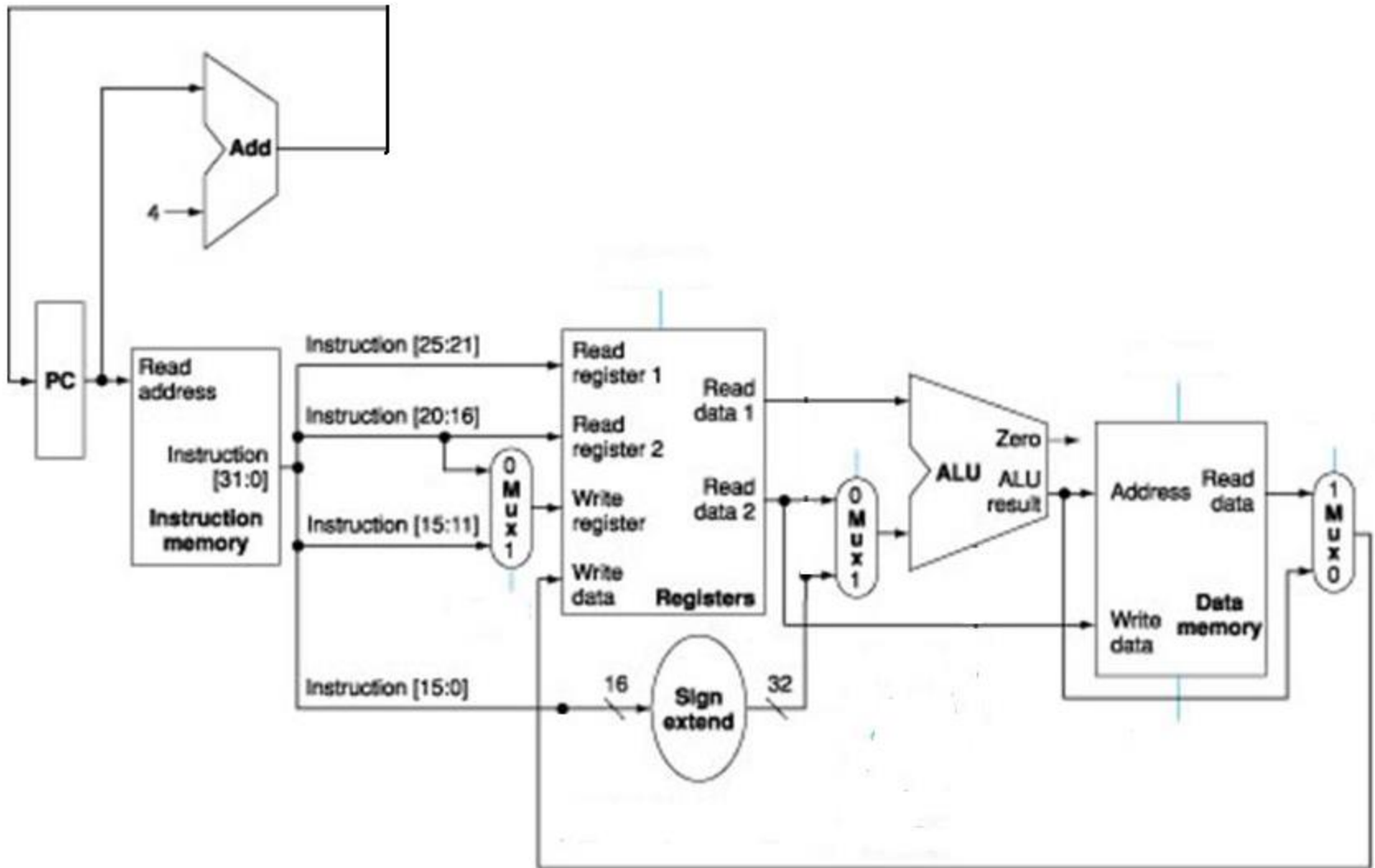

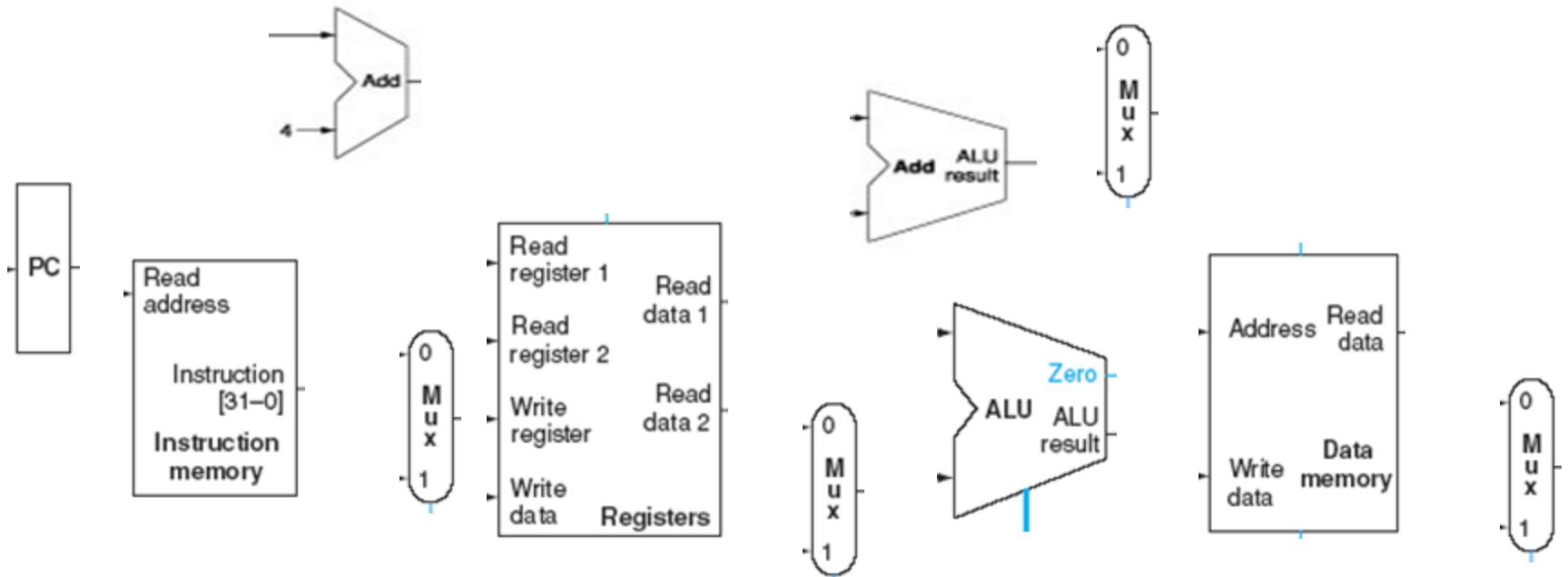
Datapath for R-type, memory, and branch operations



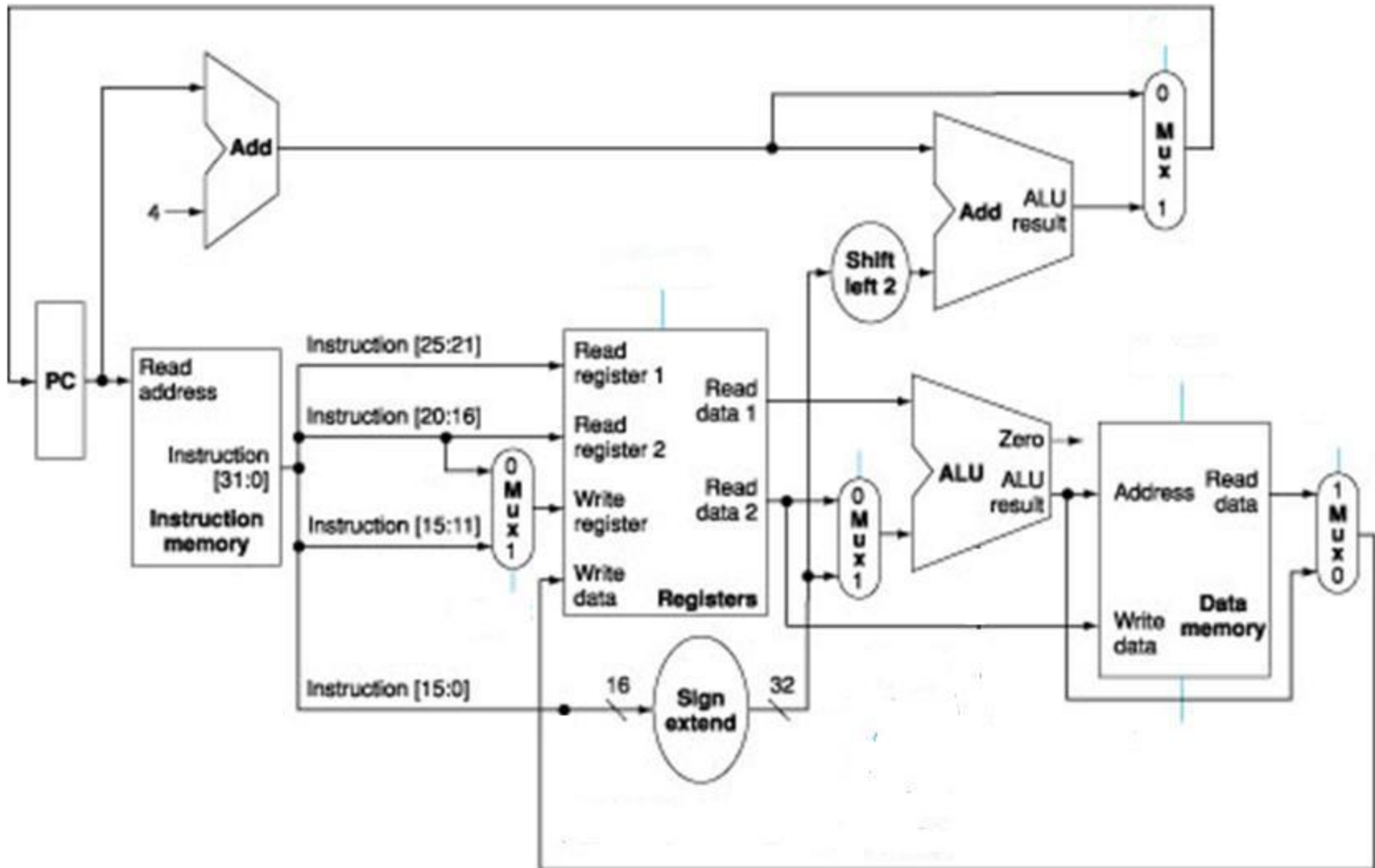Datapath for R-type, memory, and branch operations (Answer)



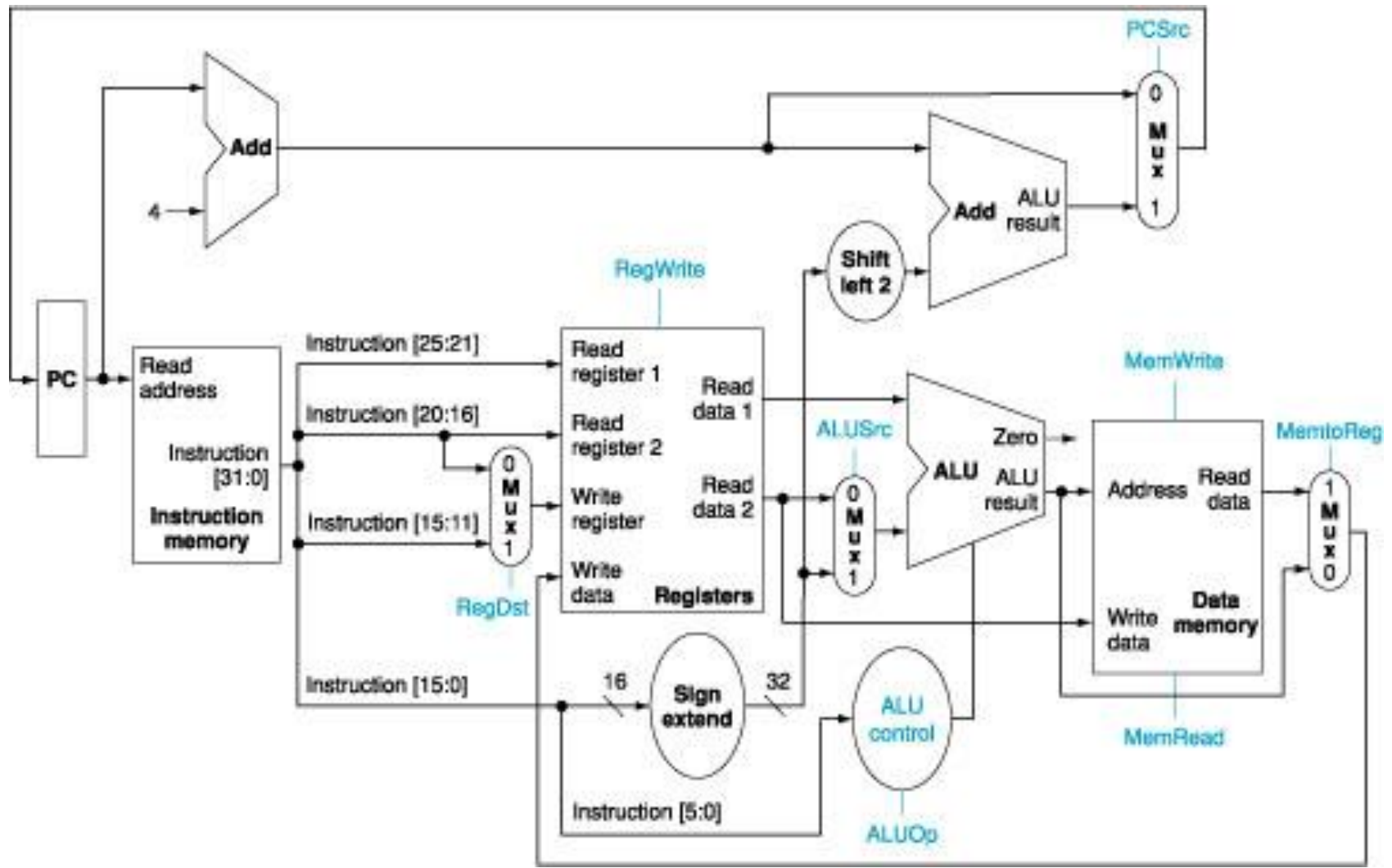Datapath for Memory, R-type and Branch Instructions, plus the control signals




Jump Instruction

- Jump instruction seems easy to implement
 - We just need to replace the lower 28 bits of the PC with the lower 26 bits of the instruction shifted by 2 bits
 - The shift is achieved by simply concatenating 00 to the jump offset


Implementing Jumps

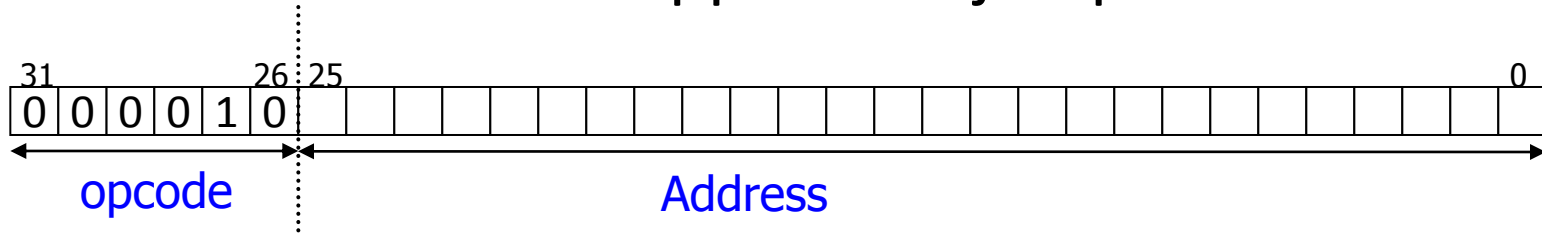- The one we have supports arithmetic/logic instructions, branch instructions, load and store instructions
 - We need also to support the jump instruction




- What are the changes we need to make?

Add j?

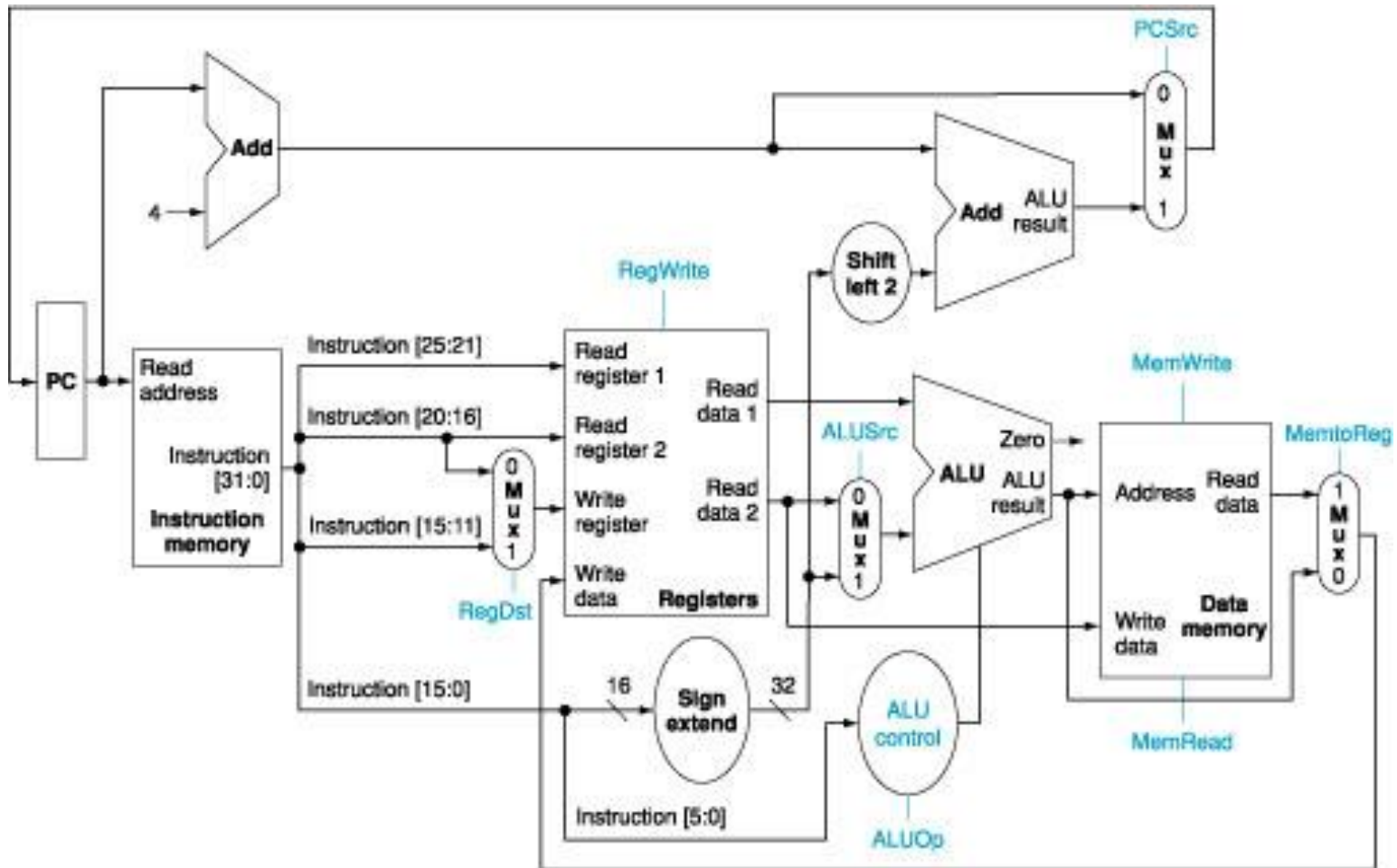

Supporting Jump Instruction

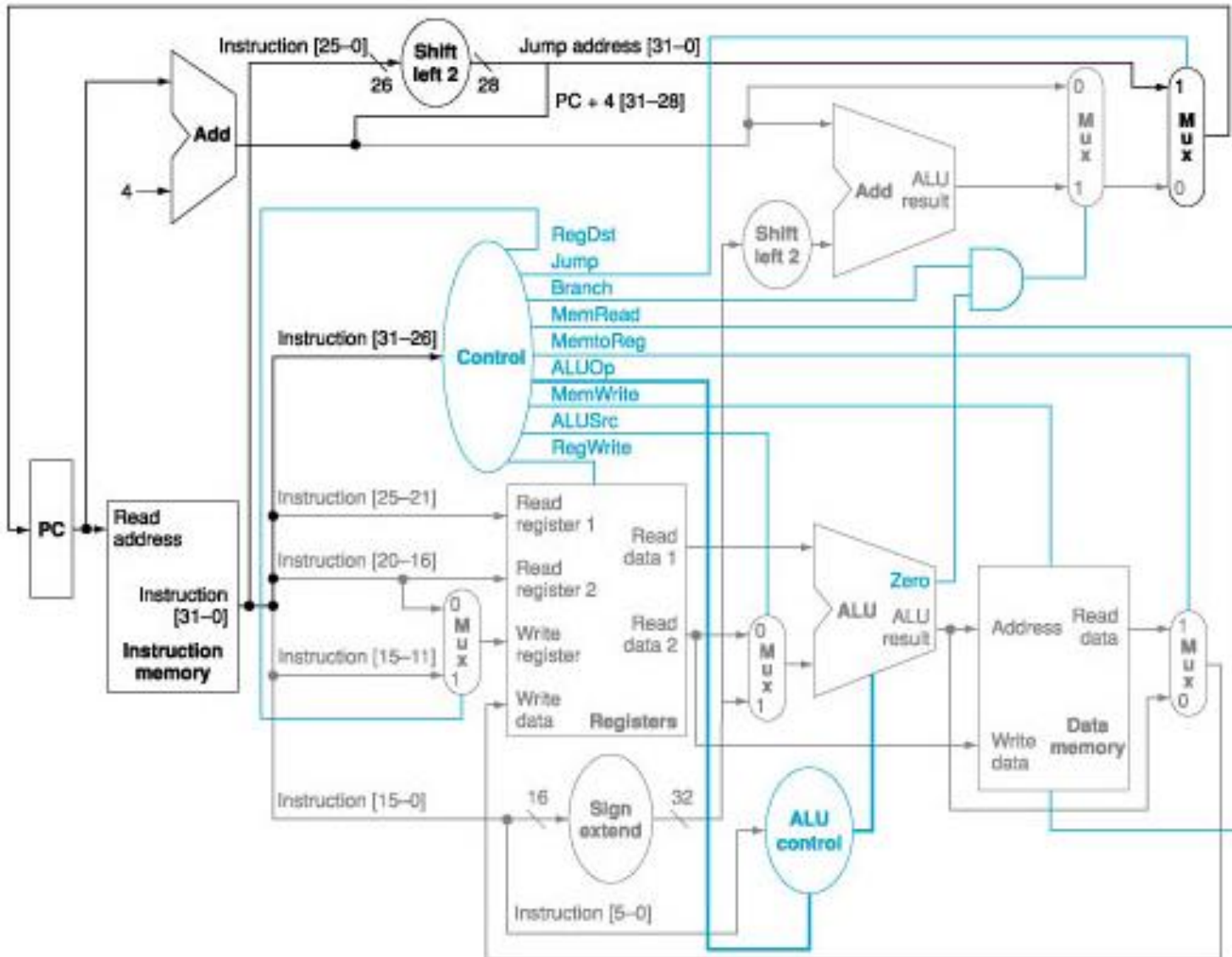

In Class Exercise