


Digital Logic

Abstractions in CS (gates)

- Basic Gate: Inverter

Truth Table

I	O
0	1
1	0

 


Abstractions in CS (gates)

- Basic Gate: AND

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


 


Abstractions in CS (gates)

- Basic Gate: NAND (Negated AND)

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  


Abstractions in CS (gates)

- Other Basic Gates: OR gate

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


Abstractions in CS (gates)

- Other Basic Gates: NOR (Negated OR) gate

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


Abstractions in CS (gates)

- Other Basic Gates: XOR gate

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 

Logic Blocks

- Logic blocks are built from gates that implement basic logic functions
 - Any logical function can be constructed using AND gates, OR gates, and inversion.

Adder

- In computers, the most common task is add.
- In MIPS, we write “add \$t0, \$t1, \$t2.”
The hardware will get the values of \$t1 and \$t2, feed them to an adder, and store the result back to \$t0.
- So how the adder is implemented?

Half-adder

- How to implement a one-bit half-adder with logic gates?
- A half adder takes two inputs, a and b, and generates two outputs, sum and carry. The inputs and outputs are all one-bit values.



Half-adder

- First, how many possible combinations of inputs?

Half-adder

- Four combinations.

a	b	sum	carry
0	0		
0	1		
1	0		
1	1		

Half-adder

- Four combinations.

Index = \sum inputs	a	b	sum	carry
0	0	0		
1	0	1		
2	1	0		
3	1	1		

Half-adder

- The value of sum should be? Carry?

a	b	sum	carry
0	0		
0	1		
1	0		
1	1		


Half-adder

- Okay. We have two outputs. But let's implement them one by one.
- First, how to get sum? Hint: look at the truth table.

a	b	sum
0	0	0
0	1	1
1	0	1
1	1	0

Half-adder

- Sum

 


How about carry?

- The truth table is

a	b	carry
0	0	0
0	1	0
1	0	0
1	1	1


Carry

- So, the circuit for carry is

 


Half-adder

- Put them together, we get

 

1-Bit Adder

 - 1-bit full adder
 - Also called a (3, 2) adder



Constructing Truth Table for 1-Bit Adder

Inputs			Outputs	
a	b	CarryIn	CarryOut	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Truth Table for a 1-Bit Adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Sum?

- Sum is `1` when one of the following four cases is true:
 - $a=1, b=0, c=0$
 - $a=0, b=1, c=0$
 - $a=0, b=0, c=1$
 - $a=1, b=1, c=1$

Sum

- The idea is that we will build a circuit made of **and** gates and an **or** gate **faithfully** according to the truth table.
 - Each and gate corresponds to one “true” row in the truth table. The and gate should output a “1” if and only if the input combination is the same as this row. In all other cases, the output is “0.”
 - So, whenever the input combination falls in one of the “true” rows, one of the and gates is “1”, so the output of the or gate is 1.
 - If the input combination does not fall into any of the “true” rows, none of the and gates will output a “1”, so the output of the or gate is 0.

Boolean Algebra

- We express logic functions using logic equations using Boolean algebra
 - The OR operator is written as $+$, as in $A + B$.
 - The AND operator is written as \cdot , as $A \cdot B$.
 - The unary operator NOT is written as \bar{A} or A' .
- **Remember: This is not the binary field. Here $0+0=0$, $0+1=1+0=1$, $1+1=1$.**

Sum


a=1, b=0, c=0

a=0, b=1, c=0

a=0, b=0, c=1

a=1, b=1, c=1
 
$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$



Carryout bit?

- Carryout bit is also '1' in four cases. When a, b and carryin are 110, 101, 011, 111.


$$CO = (a \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot c) + (a \cdot b \cdot c)$$

- Does it mean that we need a similar circuit as sum?


Carryout bit

$$CO = (a \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot c) + (a \cdot b \cdot c)$$

 - Actually, it can be simpler $CO = (a \cdot b) + (b \cdot c) + (c \cdot a)$





1-Bit Adder

 

Delay

  - Hardware has delays.
- Delay is defined as the time since the input is stable to the time when the output is stable.
- How much more delay does the one-bit full adder take, when compared to the one-bit half adder?



32-bit adder

- How to get the 32-bit adder used in MIPS?

32-bit adder

