

Digital Circuits

Review – Getting the truth table

- The first step in designing a digital circuit usually is to get the truth table.
- That is, for **every** input combination, figure out what an output bit should be, and write them down in a table.

Review – From the truth table to circuits

- Any truth table can be translated into a circuit consisting of several **and** gates followed by one **or** gate.
 - It means that any function can be implemented in this way
- Call a row in the truth table in which the output is `1' a ``true row'' and the input combination in this row a ``true input combination'' or just a ``true combination.''
- Each **and** gate corresponds to one ``true row'' in the truth table. The **and** gate should output a `1' if and only if the input combination is the same as this row. In all other cases, the output of this **and** gate is `0.'
 - So, whenever the input combination is the same as one of the ``true combinations,''' one of the **and** gates outputs `1'', so the output of the **or** gate is 1.
 - If the input combination is not the same as any of the ``true combinations,''' none of the **and** gates will output a `1'', so the output of the **or** gate is 0.

Logic Functions

- Drawing circuits is ... Usually we express logic functions using logic equations which are more succinct and carry the same information
 - The OR operator is written as $+$, as in $A + B$.
 - The AND operator is written as \cdot , as $A \cdot B$.
 - The unary operator NOT is written as \bar{A} or A' .
- **Remember:** This is **NOT** the binary field. Here $0+0=0$, $0+1=1+0=1$, $1+1=1$.

Logic functions

- For example, the sum in the one-bit full adder is

$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$

- From a logic function you can immediately know what the circuit looks like.
- Truth table == Circuits == Logic function, equivalent.
- So we are going to get familiar with getting the logic functions from the truth table

Problems

- Ex 1. Assume that X consists of 3 bits, $x_2 x_1 x_0$. Write a logic function that is true if and only if X contains only one 0

EX 1

X2	X1	X0	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

EX 1

X2	X1	X0	output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Ex 1

- Output = $x_2x_1x_0' + x_2x_1'x_0 + x_2'x_1x_0$

Ex 2

- Assume that X consists of 3 bits, $x_2 x_1 x_0$.
Write a logic function that is true if and only if X contains an even number of 0s.

EX 2

X2	X1	X0	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

EX 2

X2	X1	X0	output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Ex 2

- Output = $x_2x_1'x_0' + x_2'x_1'x_0 + x_2'x_1x_0' + x_2x_1x_0$

Ex 3

- Assume that X consists of 3 bits, $x_2 x_1 x_0$.
Write a logic function that is true if and only if X when interpreted as an unsigned binary number is no less than 5.

Ex 3

X2	X1	X0	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Ex 3

X2	X1	X0	output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Ex 3

- Output = $x_2x_1'x_0 + x_2x_1x_0' + x_2x_1x_0$

The Karnaugh Map

Simplifying Digital Circuits


- Reconsider the 1-bit full adder. The carry bit is

$$CO = (a \cdot b \cdot \bar{c}) + (a \cdot \bar{b} \cdot c) + (\bar{a} \cdot b \cdot c) + (a \cdot b \cdot c)$$

- But we can implement the function with a much simpler circuit:

$$CO = (a \cdot b) + (b \cdot c) + (c \cdot a)$$

- How to get there?

 

Simplifying digital circuit

- There are many methods.
 - Using boolean algebra
 - Using K-map
 - By just being really smart...

Boolean Algebra Laws

- Identity Law:
 - $A + 0 = A$
 - $A * 1 = A$
- Zero and One Laws:
 - $A + 1 = 1$
 - $A * 0 = 0$
- Inverse Laws:
 - $A + \bar{A} = 1$
 - $A * \bar{A} = 0$
- $A * \bar{A} = 0$
- Commutative Laws:
 - $A + B = B + A$
 - $A * B = B * A$
- Associative Laws:
 - $A + (B + C) = (A + B) + C$
 - $A * (B * C) = (A * B) * C$
- Distributive Laws:
 - $A * (B + C) = (A * B) + (A * C)$
 - $A + (B * C) = (A + B) * (A + C)$
- $A + A = A$

Boolean Algebra

- To use Boolean algebra, note that $CO = abc' + ab'c + a'bc + abc$
- Now,
 - $abc' + abc = ab(c' + c) = ab.$
 - $ab'c + abc = ac(b' + b) = ac$
 - $a'bc + abc = bc(a' + a) = bc$
 - We used term abc three times because $abc = abc + abc + abc!$

K-map

- It is actually more convenient to use K-map to simplify digital circuits.
- K-map is a very mechanical procedure. Nothing fancy.
- It basically uses two rules: $A+A=A$, and $AB+AB'=A$.

K-map

- K-map

c \ ab	00	01	11	10
0	0	0	1	0
1	0	1	1	1

- $CO = ab + ac + bc$

K-map rules

- Draw the K-map. Remember to make sure that **the adjacent rows/columns differ by only one bit.**
- According to the truth table, write 1 in the boxes.
- Draw a circle around a rectangle with all 1s. **The rectangle must have size 1,2,4,8,16...** Then, reduce the terms by writing down the variables whose values do not change.
 - For example, if there is a rectangle with two 1s representing $ab'c'$ and $ab'c$, you write a term as ab' .
- Note that
 - **A term may be covered in multiple circles!**
 - **The rectangle can wrap-around!**
- Simplify to the simplest circuits possible:
 - The circle should be as large as possible.
 - Try to get the minimum number of circles, i.e., minimum number of terms in the equation.

K-map

- $F = a'bc' + a'bc + a'b'c + ab'c$

c \ ab	00	01	11	10
0	0	1	0	0
1	1	1	0	1

K-map

- $F = a'bc' + a'bc + a'b'c + ab'c$

c \ ab	00	01	11	10
0	0	1	0	0
1	1	1	0	1

The K-map is a 2x4 grid. The top row (c=0) is shaded dark blue, and the bottom row (c=1) is shaded light blue. The cell at (c=0, ab=01) containing '1' is circled in orange. Blue lines indicate groupings: a horizontal line under the first two cells of the bottom row, a horizontal line under the last two cells of the bottom row, and a vertical line around the '1' in the top row.

- $F = a'b + b'c$

K-map

- $F = a'bc' + a'bc + abc' + abc + a'b'c$

c \ ab	00	01	11	10
0	0	1	1	0
1	1	1	1	

K-map

- $F = a'bc' + a'bc + abc' + abc + a'b'c$

c \ ab	00	01	11	10
0	0	1	1	0
1	1	1	1	

- $F = b + a'c$

K-map

- $F = a'bc'd + a'bcd + abc'd + abcd + a'b'c'd + abcd'$

cd \ ab	00	01	11	10
00				
01	1	1	1	
11		1	1	
10			1	

K-map

- $F = a'bc'd + a'bcd + abc'd + abcd + a'b'c'd + abcd'$

cd \ ab	00	01	11	10
00				
01	1	1	1	
11		1	1	
10			1	

- $F = bd + a'c'd + abc$